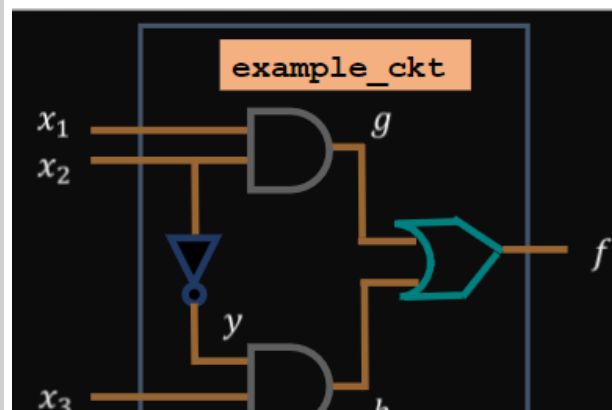


Structural Representation

```

module example_ckt(f, x1, x2,
x3);
    input x1, x2, x3;
    output f;
    and(g, x1, x2);
    not(y, x2);
    and(h, y, x3);
    or(f, g, h);
endmodule


```



and(g,x1,x2); g=x1&x2

Behavioral Representation

```
module example_ckt(f, x1, x2, x3);
    input x1, x2, x3;
    output f;
    assign f = (x1 & x2) | (~x2 & x3);
endmodule
```

 

Bitwise operators:

- ☐ $\sim A$ =This will produce 1's complement of A
- ☐ $-A$ =This will produce 2's complement of A
- ☐ $A \& B$ =Bitwise AND
- ☐ $A | B$ =Bitwise OR
- ☐ $A \wedge B$ =Bitwise XOR
- ☐ $A \wedge \sim B$ / $A \sim \wedge B$ =Bitwise XNOR
- ☐ $!A$ =NOT A(!A)produces "1(True)" only if all bits of A are 0 else !A gives "0(False)"
- ☐ $A \&\& B$ =The result of $A \&\& B$ is "1(True)" if both A and B are nonzero
- ☐ $A || B$ = $A || B$ gives "1(True)" unless both A and B are zero
- ☐ $A+B$ =Addition of two single or multi bit numbers
- ☐ $A-B$ =Subtraction of two single or multi bit numbers
- ☐ $A*B$ =Multiplication of two single or multi bit numbers
- ☐ A/B =Division of of two single or multi bit numbers
- ☐ $A\%B$ =This returns the remainder of the integer division A/B
- ☐ $A==B$ =1(True) if A is equal to B,0(False)otherwise
- ☐ $A!=B$ =1(True) if A is not equal to B,0(False)otherwise
- ☐ $A>B$ =1(True) if A is greater than B,0(False)otherwise
- ☐ $A<B$ =1(True) if A is less than B,0(False)otherwise
- ☐ $>>$ =Shift right logical (division by 2)
- ☐ $<<$ =Shift left logical(multiplication by 2)

- {} =join bits
- {n{m}} =Duplicate m,n times
- D=A?B:C = D is equal to B if A is true,otherwise D is equal to C

```

module example(a, b);
input b;
output a;
wire [7:0] in1, in2; // 8-bit wire type
variables
reg [0:31] base_clk; // 32-bit reg type
variable
assign a = in1[7] * in2[2];
endmodule

```

wire a,b; //wire declaration,changes continuously

reg clock; //register declaration,does not changes continuously

wire[7:0] in1,in2 //8 bit wire type variables wire[7]=MSB

reg[0:31] base_clk; //32 bit wire type variables

reg[7:0] mem[15:0]; //mem is an array has 16 column

reg[7:0] mem[7:0][15:0]; //mem is an array has 8 row 16 column


parameter n=5; //declaring constant

```

module full_add(S, Cout, A, B, Cin);
// This module implements a 1-bit full adder
input A, B, Cin;
output S, Cout;

assign S = A ^ B ^ Cin;
assign Cout = (A & B) | (Cin & (A ^ B));
endmodule

```

 

```

always @ (sensitivity_list)
[begin]
    [procedural assignment statements]
    [if-else statements]
    [case statements]
    [while, repeat and for loops]
[end]

```

```

always @ (*)
    if(expression1)
    begin
        statement;
    end
    else if(expression2)
    begin
        statement;
    end
    else
    begin
        statement
    end
end

```

```

module mux2to1(A, B, S, Z);

    input A, B, S;
    output reg Z;

    always @ (A, B, S)
    begin
        if(S == 0)
            Z = A;
        else
            Z = B;
        end
    endmodule

```

4-Bit Ripple Carry Adder

```

module fulladd4(S0, S1, S2, S3, Cout, A0, A1, A2, A3, B0, B1, B2, B3, Cin);
    input A0, A1, A2, A3, B0, B1, B2, B3, Cin;
    output S0, S1, S2, S3, Cout;
    wire Cout0, Cout1, Cout2;
    fulladd stage0 (S0, Cout0, A0, B0, Cin);
    fulladd stage1 (S1, Cout1, A1, B1, Cout0);
    fulladd stage2 (S2, Cout2, A2, B2, Cout1);
    fulladd stage3 (S3, Cout, A3, B3, Cout2);
endmodule

module fulladd(S, Cout, A, B, Cin);
    // This module implements a 1-bit full adder
    input A, B, Cin;
    output S, Cout;

    assign S = A ^ B ^ Cin;
    assign Cout = (A & B) | (Cin & (A ^ B));
endmodule

```